Computer Architecture

Hossein Asadi
Department of Computer Engineering
Sharif University of Technology
asadi@sharif.edu

Lecture 3   1

Today's Topics

- Register Transfer Language (RTL)

Lecture 3   Sharif University of Technology, Spring 2021   2

Copyright Notice

Lecture 3   Sharif University of Technology, Spring 2021   3

Data Movements in Digital Systems

- Digital Systems Consists of
  - Combinational logic
    - AND gate, OR gate, NOT gate, etc
  - Sequential elements
    - FFs, latches
- Question:
  - How we can describe data movements in digital systems?
    - Gate-level?
      - Too much details and very complicated

Lecture 3   Sharif University of Technology, Spring 2021   4

RTL & Micro-Operation

- Data Movement Characterized in terms of:
  - Registers
    - Set of flip-flops/latches
  - Operations done on registers
- Register Transfer Language (RTL)
  - Data movement at register level
  - A language to describe behavior of computers in register flow format
- Micro-operation (Micro-ops or uOps)
  - Functions performed on registers
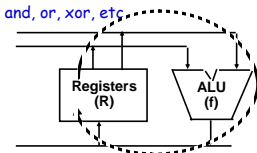   - Shift, clear, load, increment, etc.

Lecture 3   Sharif University of Technology, Spring 2021   5

Micro-Operation

- Definition:
  - An elementary operation performed on information stored in one or more registers
    - During one clock pulse
  - R ← F(R,R)
    - F: shift, load, clear, and, or, xor, etc.

Lecture 3   Sharif University of Technology, Spring 2021   6

1

High-Level Description of Computer uArch

- In Terms of RTL & uOps:
  - Set of registers and their functions
  - Microoperations set
    - Set of allowable uops provided by uArch
  - Control signals that initiate sequence of uOps to perform functions

Register Transfer Language

- Our Focus in RTL
  - System's registers
  - Data transfers between them
  - Data transformations in them

Designation of Registers

- How Registers Designated?
  - Using capital letters
  - Sometimes followed by numbers
    - e.g., A, R13, IR
- Often names indicate function:
  - PC
    - Program Counter
  - IR
    - Instruction Register
  - MAR
    - Memory Address Register

Designation of Registers (cont.)

- How Registers Represented?
  - Registers and their contents can be viewed and represented in *various ways*
  - A register can be viewed as a single entity:

MAR

  - Registers may also be represented showing bits of data they contain

Designation of Registers (cont.)

- How Registers Represented?
  - Common ways of drawing the block diagram of a register

Register

R1

Showing individual bits

7	6	5	4	3	2	1	0

15   0

R2

Numbering of bits

15   8 7   0

PC(H)	PC(L)

Subfields
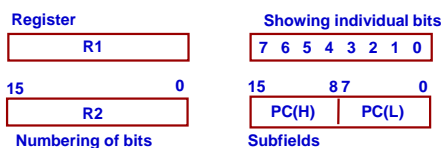
Data Transfer

- Data Transfer:
  - Copying contents of one reg to another reg
- Example:
  - R2 ← R1
  - Contents of R1 copied (loaded) into R2
  - A simultaneous transfer from R1 to R2
    - All bits transferred at same time on one clock cycle
    - R1: source, R2: destination
    - Data lines from R1 to R2
  - This is a non-destructive
    - Contents of R1 not altered by copying them to R2
  - Control lines to perform action

Data Transfer (cont.)

- Controlled (Conditional) Data Transfer
  - Actions will occur if a certain condition is true
  - Similar to an "if" statement in SW programming
  - Represented as:

  P: R2 ← R1

  "if P = 1, then load contents of R1 into R2",
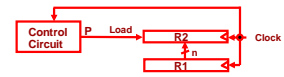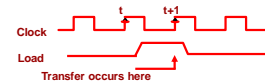 i.e., if (P = 1) then (R2 ← R1)

Controlled Data Transfer

- HW Implementation

  P: R2 ← R1

  Block diagram

  Timing diagram

  •**Registers assumed to use *positive-edge-triggered* flip-flops**

Data Transfer (cont.)

- Simultaneous Micro-operations
  - If two or more operations are to occur simultaneously, they are separated with commas

  P: R3 ← R5, MAR ← IR

- Here, if control function P = 1 ➜
  - Load contents of R5 into R3
  - At same clock, load contents of IR into MAR

Data Transfer (cont.)

- Practice
  - Draw hardware implementation of following statement
  - P: R1 ← R2, R2← R1

Blocking and Non-Blocking Statements in RTL

- Non-Blocking Statements
  - Statement scheduled and executed together with other non-blocking assignments
  - Example in Verilog
    - A <= B
    - B <= C
- Blocking Statements
  - Statement executed sequentially
  - Example in Verilog
    - A = B
    - B = C

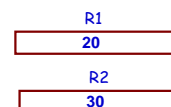## Practice

- Code1
  - R1 ← R2, R2 ← R1
- Code2
  - R1 ← R2
  - R2 ← R1
- Code3
  - R1 <= R2
  - R2 <= R1
- Question:
  - New values of R1 and R2?

R1
20

R2
30

3

Common Micro-Ops

- **Transfer** (R0 ← R1)
  - Transfers data from a reg to another reg
- **Arithmetic** (R0 ← R1 + R2)
  - Performs arithmetic on data in registers
- **Logic/Bit Manipulation**
  - Performs bit (Boolean) operations on data
    R0 ← R1 & R2 ; or R0 ← R1 | R2
- **Shift**
  - Shift data in regs by n bits positions
    R0 ← R1 << 3; or R0 ← R2 >> 2

RTL & MIPS Assembly

MIPS Code	RTL Code
add $t0, $s2, $s4	$t0 ← $s2 + $s4
and r1, r2, r3	r1 ← r2 ^ r3
lw $s1, 100($s2)	$s1 ← Mem[$s2 + 100]
sw $s1, 100($s2)	Mem[$s2 + 100] ← $s1

Summary of Reg Transfer & Micro-Ops

A ← B	Transfer content of reg. B into reg. A
AR ← DR(AD)	Transfer content of AD portion of reg. DR into reg. AR
A ← constant	Transfer a binary constant into reg. A
ABUS ← R1,	Transfer content of R1 into bus A and, at the same time,
R2 ← ABUS	Transfer content of bus A into R2
AR	Address register
DR	Data register
M[R]	Memory word specified by reg. R
M	Equivalent to M[AR]
DR ← M	Memory *read* operation: transfers content of memory word specified by AR into DR
M ← DR	Memory *write* operation: transfers content of DR into memory word specified by AR

Summary of Reg Transfer & Micro-Ops (cont.)

- GPR[rs]
  - General Purpose Registers
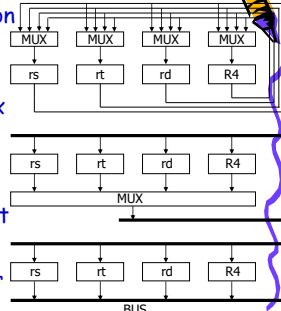 - A register from Register File indicated by index rs
- RF[rs]
  - Register File

Register Transfers: Interconnect

- **Point-to-Point Connection**
  - Dedicated wires
  - Muxes on inputs of each register
- **Common Input from mux**
  - Load enables for each register
  - Control signals for multiplexer
- **Common Bus with Output Enables**
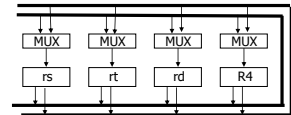 - Output enables and load enables for each register

Register Transfer: Multiple Busses

- One transfer per bus
- Each set of wires can carry one value
- **State Elements**
  - Registers
  - Register files
  - Memory
- **Combinational Elements**
  - Busses
 - ALUs
  - Memory (read)

Connecting Registers

- How to Connect 32 Registers to each other?
  - Impractical to have data and control lines to directly allow each register to be loaded with contents of every possible other registers
- To completely connect n registers
  - → n(n-1) lines
  - $O(n^2)$ cost
  - Not a realistic approach to use in a large system

Connecting Registers

- Point-to-Point Connection
  - Dedicated wires
  - Muxes on inputs of each register
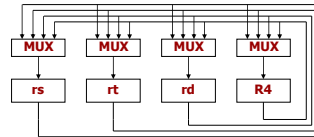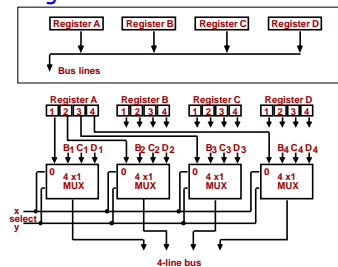
Connecting Registers (cont.)

- **Instead, Take a Different Approach**
  - One centralized set of circuits for data transfer, called bus
  - Have control circuits to select:
    - Which reg as source
    - Which reg as destination
- Bus Definition:
  - A path (of a group of wires) over which information is transferred, from any of several sources to any of several destinations
  - A group of wires with multiple drivers

Bus Transfer

- From a register to bus: BUS ← R

Bus Transfer: Bus to Destination Reg

Three-State Bus Buffers

Normal input A → Output Y=A if C=1
Control input C → High-impedence if C=0

3-State Buf vs Mux implementation
Pros: area efficient & more scalable
Cons: probably more power consumption (leakage current in high-Z)
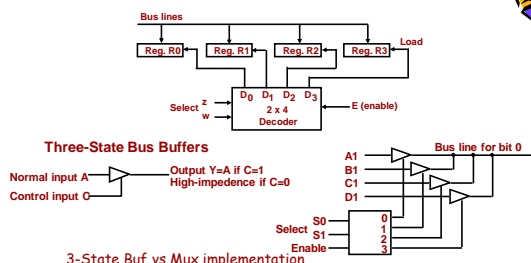
Bus vs. Point-To-Point

- Pros (Advantages)
  - Much less routing
  - Less area
  - Easy to scale
- Cons (Disadvantages)
  - Only one data transfer per clock cycle

Memory & Memory Transfer

- Memory (RAM)
  - Can be thought as a sequential circuit containing some number of registers
- Assume RAM with $r = 2^k$ Words
  - n data input lines
  - n data output lines
  - k address lines
 - A read control line
  - A write control line
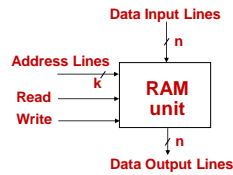
Data Input Lines
n
Address Lines
k
Read
Write
RAM unit
n
Data Output Lines

Memory & Memory Transfer (cont.)

- Memory Transfer
  - Memory viewed at register level as a device (M)
  - Should specify which address in memory
    - Since it contains multiple locations
- Memory Accesses
  - Provide target address in a special register
    - Memory Address Register (MAR, or AR)
  - Contents of MAR sent to memory address lines
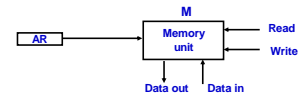
M
AR
Memory unit
Read
Write
Data out **Data in**

Memory & Memory Transfer (cont.)

- Memory Read
  - To read a value from a location in memory and load it into a register
  - RTL notation looks like this:

      MAR ← Address
      R1 ← M[MAR]

Memory & Memory Transfer (cont.)

- Memory Write
  - To write a value from a reg to a location in memory
  - RTL notation looks like this:

      MAR ← address
      M[MAR] ← R1

RTL Example

- Memory Buffer Register
  - MBR
- Accumulator
  - AC
- Program Counter
  - PC
- Memory Address Register
  - MAR
- Instruction Register
  - IR The Essentials of Computer Organization & Architecture, by L. Null and J. Lobur, 2003

Main Memory · MAR · PC · MBR · ALU · AC · InREG · OutREG · IR · 16-bit bus
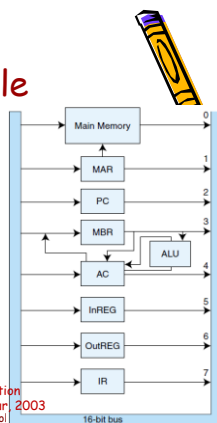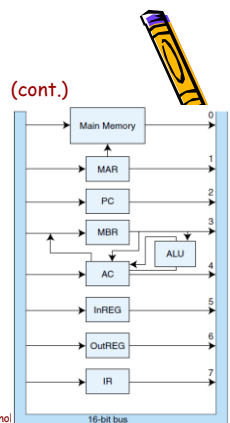
RTL Example (cont.)

- Store X
  - MAR ← X, MBR ← AC
  - M[MAR] ← MBR
- Add X
  - MAR ← X
  - MBR ← M[MAR]
  - AC ← AC + MBR

Main Memory · MAR · PC · MBR · ALU · AC · InREG · OutREG · IR · 16-bit bus

Practice

- What is RTL description of this circuit?
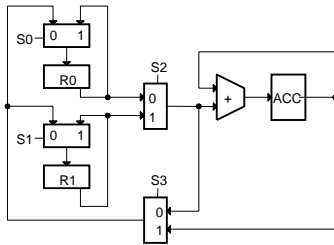
Practice (cont.)

- In Each Clock Cycle:
  - ~S3.~S2.~S1: R1 ← R0
  - ~S3.S2.~S0: R0 ← R1
  - S3.~S2.~S1: ACC ← R0 + ACC
  - S3.S2.~S0: ACC ← R1 + ACC
  - What else?
    - R1 ← ACC
    - …
- Or use "if-then-else"
  - If (S3=1 and S1=0) then …

Backup